
Cincuite Logice un Sisole si Tromzistoone Poorta Si- Nu un Deplosere de Nivelpin Diode

(1) Scopul lucranii Se va realiza un

Se va realiza un chauit Si-Mu an diode si transistorne an deplasare de nivel prin diode. Se vos másura in continuare parametria statici si dinamici ai circuitului realizat.

## 3 Functionorea porti

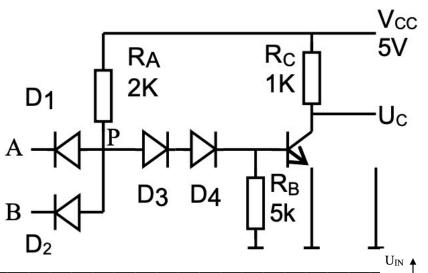

Α	В	$V_{P}$	$V_{BE}$	F
0	0	0,95	0	1
0	1	0,95	0	1
1	0	0,95	0	1
1	1	2,25	0,75	0

